

# Logic and Computer Design Fundamentals

---

## Term Review

Ming Cai

cm@zju.edu.cn

College of Computer Science and Technology,  
Zhejiang University

# Previous Year's Final Exam

---

1. Fill in the blank
2. Chose the best Choice
3. **Verilog**
4. Kaunaugh Map and Optimization
5. Circuit Analysis
  - Combinational circuit
  - Sequential circuit
6. Logic Design
  - Combinational circuit
  - Sequential circuit

---

Course Review

# HIGHLIGHTS & PROBLEMS

# Chapter 4

---

- Latches and flip-flops
- Master-slave flip-flop and edge-triggered flip-flop
  - SR master-slave flip-flop
  - edge-triggered D flip-flop
- Direct inputs: preset (direct set), clear (direct reset)
- Flip-flop timing
  - Setup time, hold time, propagation delay time
  - **Timing Equations:**  $t_p = t_{\text{slack}} + (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$   
for  $t_{\text{slack}}$  greater than or equal to zero,  $t_p \geq \max (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s)$   
for all paths from flip-flop output to flip-flop input
  - **How to calculate the maximum frequency of operation of circuit?**

# Chapter 4

---

## ■ Sequential circuit analysis

- Input equation
- Next state equation
- Output equations: **Mealy model circuits, Moore model circuits**
- State table: present state, input, next state, output
- State diagram: don't-care condition

## ■ Sequential circuit design

- State diagram: **state minimization, state assignment**, don't-care condition
- State table
- Excitation equation
- Input equations (next state equations)
- Output equations
- Optimization
- Technology Mapping
- Verification

# Chapter 4

- Difference between Latches and Flip-Flops

Latch	Flip-Flop
Latches are level sensitive devices	Flip-flops are edge sensitive devices
Latches are sensitive to glitches	Flip-flops are immune to glitches
Latches take less gates and power	Flip-flops take more gates and power
Latches are faster	Flip-flops are slower

- Latches are transparent.
- Master-slave flip-flops use alternating clocks to break the path from input to output.
- S-R/J-K master-slave flip-flops have “1s catching” behavior.
- Edge-triggered flip-flops respond to the input at a well-defined moment (at the clock-transition).

# Chapter 4


---

- Three basic descriptors for flip-flops
  - Characteristic (truth) tables
  - Characteristic equations
  - Excitation tables
- Four different types of flip-flops
  - SR (S-Set, R-Reset) flip-flop
  - JK (J-Set, K-Reset) flip-flop
  - D (Data or Delay) flip-flop
  - T (Toggle) flip-flop
- Transformation among flip-flops
  - Mealy model circuits and Moore model circuits
  - Flip-Flop Conversion

# Chapter 4

 
## ■ Problem: Sequential circuit analysis

A sequential circuit has one flip-flop  $Q$ , two inputs  $x$  and  $y$ , and one output  $S$ . It consists of a full-adder circuit connected to a D flip-flop, as shown in Fig. Derive the state table and state diagram of the sequential circuit.



Present state	Inputs		Next state	Output
$Q$	$x$	$y$	$Q$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

State table

 


State diagram



# Chapter 4
 
## ■ Problem: Sequential circuit analysis

The timing parameter in the sequential circuit are as follows: AND Gate:  $t_{pd} = 7.0\text{ns}$ ; OR Gate:  $t_{pd} = 8.0\text{ns}$ ; XOR Gate:  $t_{pd} = 11.0\text{ns}$ ; Flip-flop:  $t_{pd} = 7.0\text{ns}$ ,  $t_s = 4.0\text{ns}$ ,  $t_h = 2.0\text{ns}$ . Determine the maximum frequency of operation of the circuit in megahertz (MHz).



1) find the longest path delay from clock edge to clock:


$$t_{\text{delay-clock edge to clock edge}} = \text{FF } t_{pd} + 3 * \text{AND } t_{pd} + \text{OR } t_{pd} + \text{FF } t_s = 7 + 3 * 7 + 8 + 4 = 40 \text{ ns}$$

2) determine the maximum frequency:  $f_{\text{max}} = 1/t = 25 \text{ MHz}$

# Chapter 4
 
## ■ Problem: Sequential circuit design

Design the sequential circuit specified by the state diagram in the figure using JK flip-flops.



unused states:  
101, 110, 111

Answer:

State table

<i>Present state ABC</i>	<i>Input x</i>	<i>Next state ABC</i>	<i>Output y</i>
000	0	011	0
000	1	100	1
001	0	001	0
001	1	100	1
010	0	010	0
010	1	000	1
011	0	001	0
011	1	010	1
100	0	010	0
100	1	011	1

# Chapter 4

## ■ Problem: Sequential circuit design

Design the sequential circuit specified by the state diagram in the figure using JK flip-flops.

Answer:

<i>Present state</i> <i>ABC</i>	<i>Input</i> <i>x</i>	<i>Next state</i> <i>ABC</i>	<i>Output</i> <i>y</i>	<i>Flip-flop inputs</i>					
				<i>J<sub>A</sub></i>	<i>K<sub>A</sub></i>	<i>J<sub>B</sub></i>	<i>K<sub>B</sub></i>	<i>J<sub>C</sub></i>	<i>K<sub>C</sub></i>
000	0	011	0	0	x	1	x	1	x
000	1	100	1	1	x	0	x	0	x
001	0	001	0	0	x	0	x	x	0
001	1	100	1	1	x	0	x	x	1
010	0	010	0	0	x	x	0	0	x
010	1	000	1	0	x	x	1	0	x
011	0	001	0	0	x	x	1	x	0
011	1	010	1	0	x	x	0	x	1
100	0	010	0	x	1	1	x	0	x
100	1	011	1	x	1	1	x	1	x

$$\begin{aligned}
 J_A &= B'x & K_A &= 1 \\
 J_B &= A + C'x' & K_B &= C'x + Cx' \\
 J_C &= Ax + A'B'x' & K_C &= x \\
 y &= x
 \end{aligned}$$

The machine is self-correcting because  $K_A = 1$ .

unused states:  
101, 110, 111

State table

JK flip-flop input

# Chapter 4

---

- Problem: **Sequence Detector**

Design a **Mealy model** circuit to recognize a sequence 01010011. The circuit outputs 1 to indicate a sequence 01010011 was recognized. Otherwise, the circuit outputs 0. Please derive the state diagram, state table, next state functions and output functions, and draw the circuit diagram.

- Problem: **Multiple-sequence Detector**


Design a **Moore model** circuit to recognize **two sequences** 0101 and 0011. The circuit outputs 01 to indicate a sequence 0101 was recognized and outputs 11 to indicate 0011 recognized. Otherwise, the circuit outputs 00. Please derive the state diagram, state table, next state functions and output functions, and draw the circuit diagram.

# Chapter 4

## ■ Problem: Sequence generation

Design a controllable sequence counter. When control input  $C = 1$ , counter sequence is  $000 \rightarrow 100 \rightarrow 110 \rightarrow 111 \rightarrow 011 \rightarrow 000$ ; When  $C = 0$ , sequence is  $000 \rightarrow 100 \rightarrow 110 \rightarrow 010 \rightarrow 011 \rightarrow 000$ . Please derive the state diagram, state table, next state functions and output functions, and draw the circuit diagram.

Answer:

 


State diagram

# Chapter 4

## ■ Problem: Sequence generation

Answer:

 

State diagram

Current State Q2Q1Q0	Next State	
	C = 0 Q2'Q1'Q0'	C = 1 Q2'Q1'Q0'
000	100	100
001	xxx	xxx
010	011	xxx
011	000	000
100	110	110
101	xxx	xxx
110	010	111
111	xxx	011

State table

# Chapter 4

## ■ Problem: Sequence generation

Answer:

D <sub>2</sub>		Q <sub>1</sub> Q <sub>0</sub>			
		00	01	11	10
CQ <sub>2</sub>	00	1	-	0	0
	01	1	-	-	0
	11	1	-	0	1
	10	1	-	0	-

D <sub>1</sub>		Q <sub>1</sub> Q <sub>0</sub>			
		00	01	11	10
CQ <sub>2</sub>	00	0	-	0	1
	01	1	-	-	1
	11	1	-	1	1
	10	0	-	0	-

D <sub>0</sub>		Q <sub>1</sub> Q <sub>0</sub>			
		00	01	11	10
CQ <sub>2</sub>	00	0	-	0	1
	01	0	-	-	0
	11	0	-	1	1
	10	0	-	0	-

Input equations

$$D_2 = \overline{Q_1} + C\overline{Q_0}$$

$$D_1 = Q_2 + Q_1\overline{Q_0}$$


$$D_0 = CQ_2Q_1 + \overline{Q_2}Q_1\overline{Q_0}$$

# Chapter 4
 
## ■ Problem: Sequence generation

Design a waveform generator using D flip-flops and NOR gates. The waveforms of output  $Y_0 \sim Y_2$  are shown below. Requirement:

- Draw the Moore state diagram for the circuit.
- Find the state table and make a state assignment.
- Derive the next state functions and output functions.
- Design the circuit using D flip-flops and NOR gates, draw the circuit diagram.





# Chapter 4

## ■ Problem: Flip-Flop Conversion

Construct a JK flip-flop using a D flip-flop, a two-to-one-line multiplexer, and an inverter.


Answer:

JK flip-flop characteristic equation

$$Q(t+1) = J \bar{Q} + \bar{K} Q$$

D flip-flop excitation equation
 
$$D = Q(t+1) \Rightarrow D = J\bar{Q} + \bar{K}Q$$



# Chapter 6

## ■ Register Transfer Operations (RTL)

- **Microoperations**

- Let  $R1 = 10101010$  and  $R2 = 11110000$ , then after the operation,  $R0$  becomes:

- Conditional Transfer

## ■ Register Transfer Structures

- Multiplexer-Based Transfers
- Bus-Based Transfers
- Three-State Bus
- Other Transfer Structures

## ■ Shift Registers

- Parallel Load Shift Registers
- Bidirectional Shift Register

R0	Operation
10101010	$R0 \leftarrow R1$
11111010	$R0 \leftarrow R1 \vee R2$
10100000	$R0 \leftarrow R1 \wedge R2$
01011010	$R0 \leftarrow R1 \oplus R2$
01010100	$R0 \leftarrow \text{sl } R1$

Mode Control		Register Operation
$S_1$	$S_0$	
0	0	No change
0	1	Shift down
1	0	Shift up
1	1	Parallel load


# Chapter 6

## ■ Counters


- Asynchronous/Ripple Counter
- Synchronous Counter
  - Counter with Parallel Load

Load	Count	Action
0	0	Hold Stored Value
0	1	Count Up Stored Value
1	X	Load D

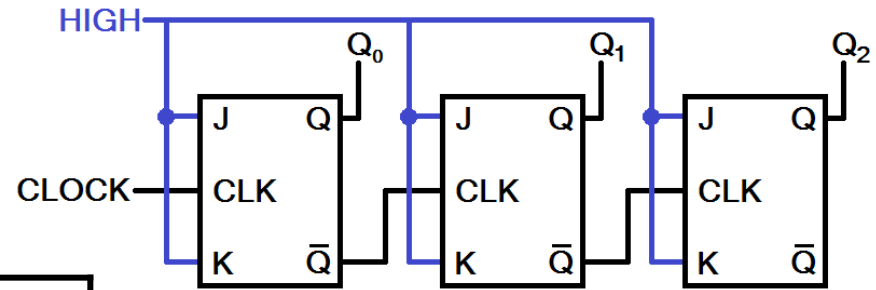- Divide-by-n (Modulo n) Counter
  - A synchronous 4-bit binary counter with a synchronous load and an asynchronous clear is used to make a Modulo 7 counter
  - How to design a Modulo-17 counter?




Asynchronous/Ripple Counter

 


Synchronous Counter
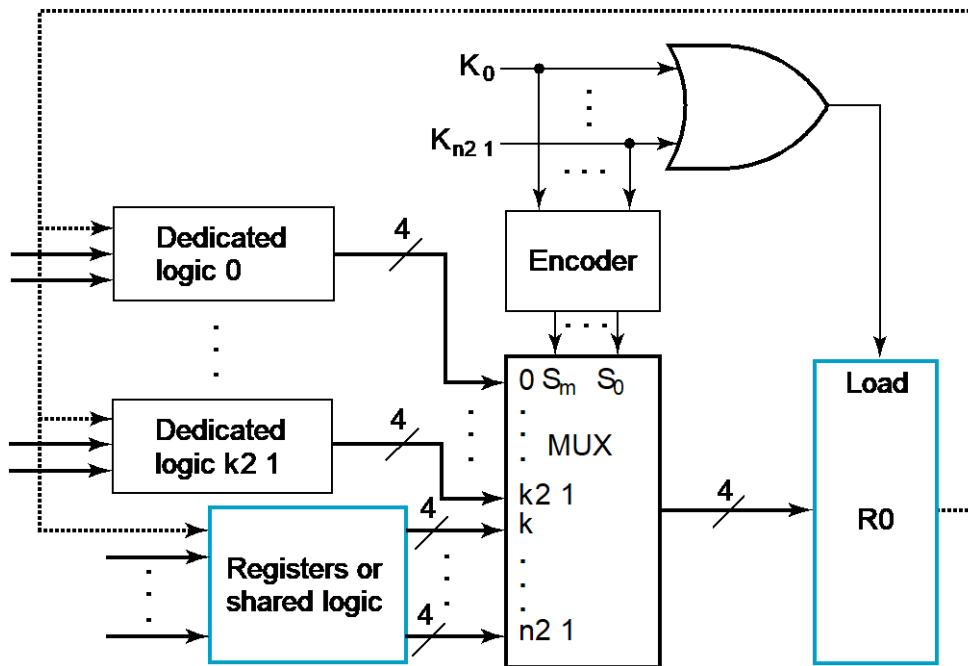
# Chapter 6

- Register Cell Design
  - Sequential Circuit Design Approach
  - Multiplexer Approach




- Serial microoperations

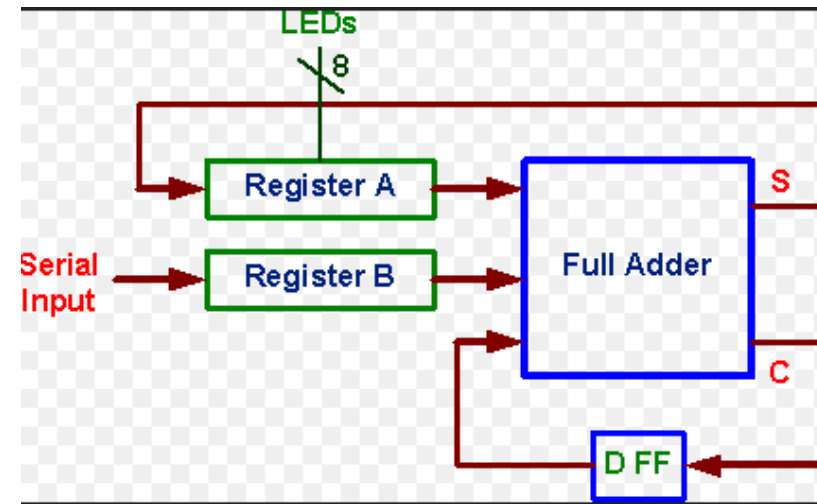

# Chapter 6


## Problem: Circuit Analysis

Shift	Load	Operation
0	0	No Change
0	1	Load
1	x	Shift down

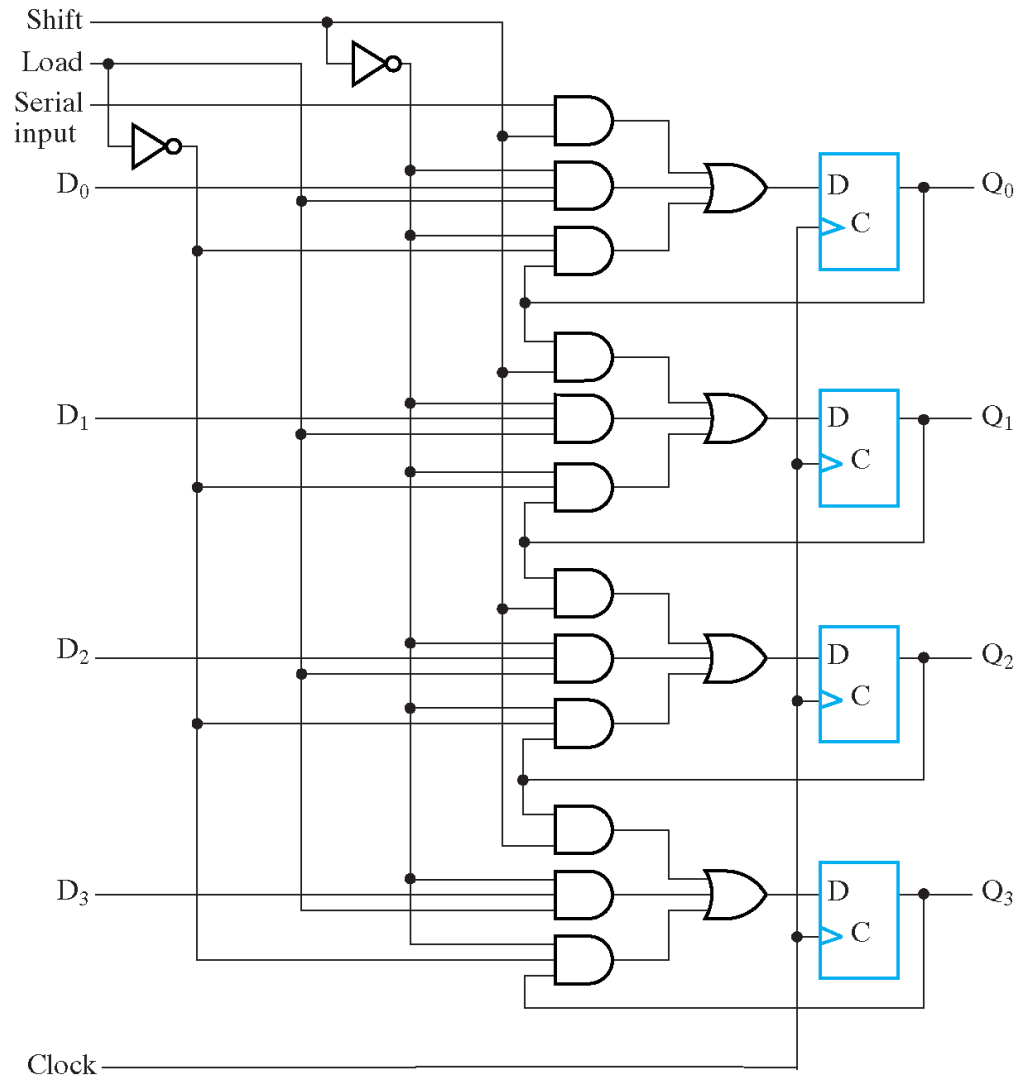


# Chapter 6

## Problem: Circuit Analysis

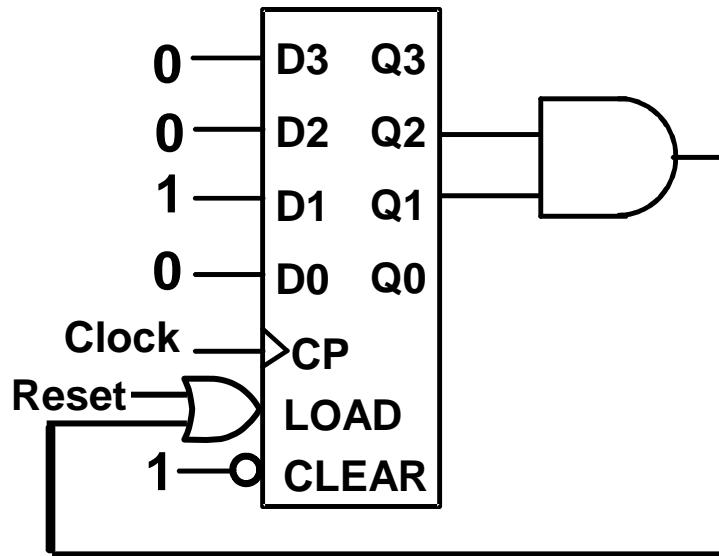

a 4-bit binary counter

0010-0110

 

a 8-bit binary counter


00001001-10000001

# Chapter 6

## ■ Problem: Circuit Analysis

Analyze the following register transfer circuit, finish the function table, and write down the corresponding register transfer operation statements in RTL forms.

C1	C2	Input Load of R1	$C_0$	Next state of R1	Function
0	0	0	0	R1	No change
0	1				
1	0				
1	1				

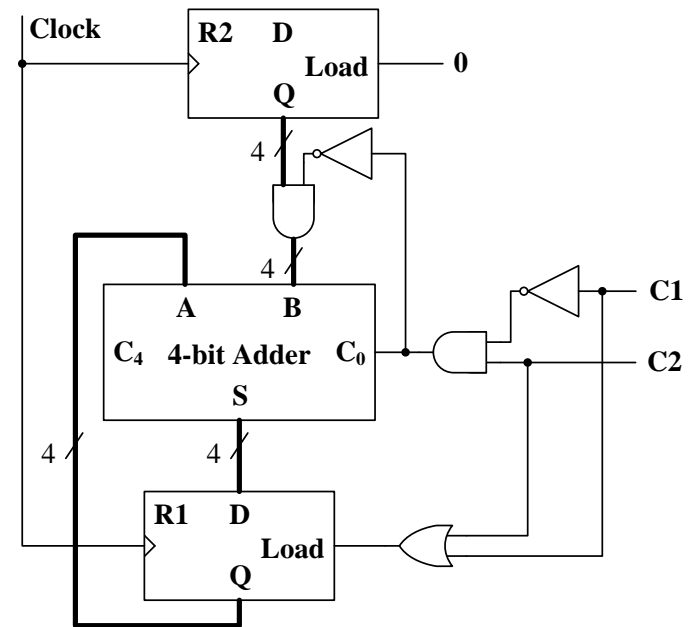

# Chapter 6


## ■ Problem: Circuit Analysis

Analyze the following register transfer circuit, finish the function table, and write down the corresponding register transfer operation statements in RTL forms.

C1	C2	Input Load of R1	C <sub>0</sub>	Next state of R1	Function
0	0	0	0	R1	No change
0	1	1	1	R1 + 1	Increment
1	0	1	0	R1 + R2	Addition
1	1	1	0	R1 + R2	Addition

**C1:  $R1 \leftarrow R1 + R2$**

**C1'C2:  $R1 \leftarrow R1 + 1$**

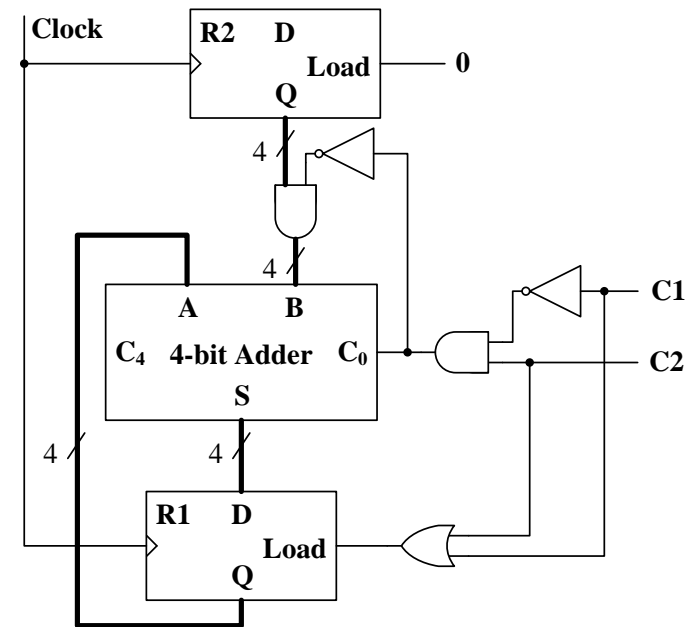



# Chapter 6

## ■ Problem: Circuit Design


A digital system has a clock generator that produces pulses at a frequency of 80 MHz. Design a circuit that provides a clock with a cycle time of 50 ns.

Answer:

The clock generator at a frequency of 80 MHz has a period of 12.5 ns.

$$50/12.5 = 4$$

 
Use a 2-bit ripple counter to count four pulses.



# Chapter 6

 
## ■ Problem: Circuit Design

Using two synchronous binary counters and logic gates to construct a minute counter that counts from BCD code “00” through BCD code “59”.



30


Answer:

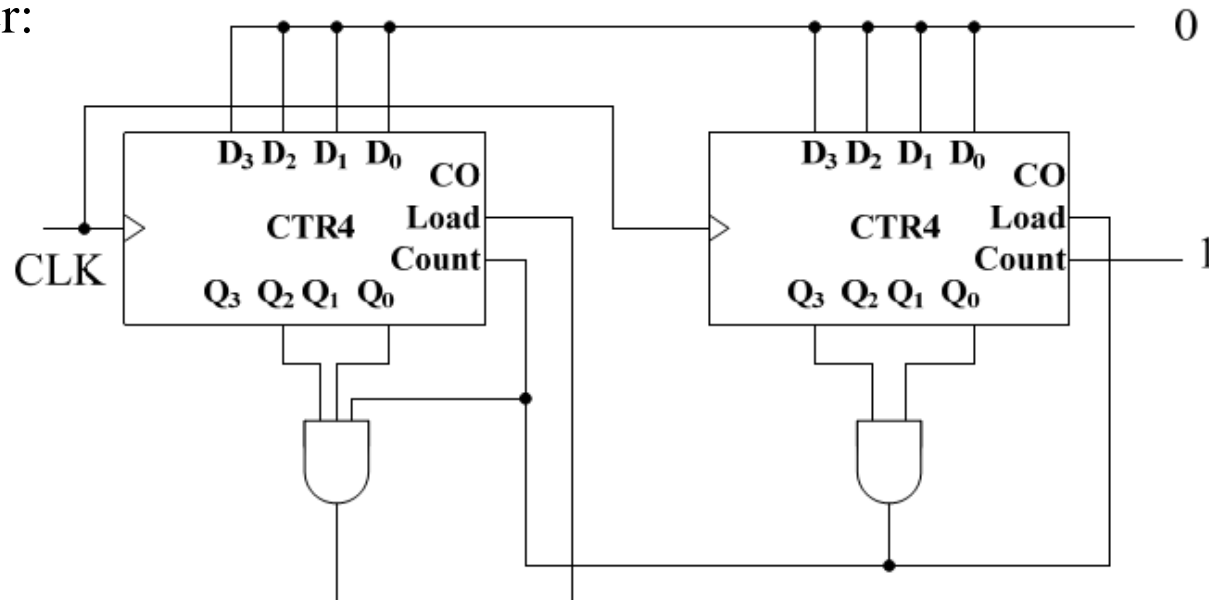

# Chapter 6

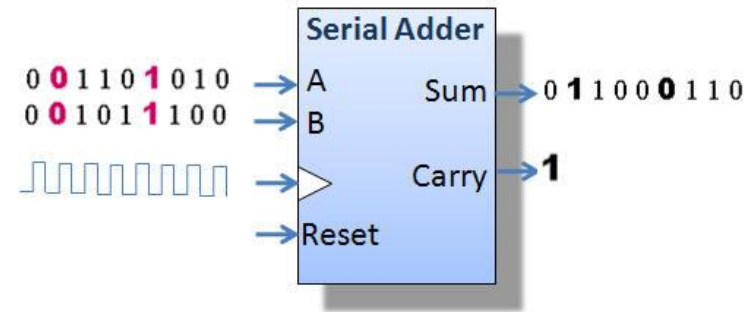
## ■ Problem: Circuit Design

How to design a serial adder by means of sequential circuit procedure?



Answer:

Present State	Inputs		Next State	Output	Flip-Flop
Q	x	y	Q	S	D
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	0	1
1	1	0	1	0	1
1	1	1	1	1	1

 

$$D = XY + (X \oplus Y)Q$$

$$S = X \oplus Y \oplus Q$$

# Chapter 6

## ■ Problem: Circuit Design

Design a serial 2's complemener with a shift register and a JK flip-flop. The binary number is shifted out from one side and it's 2's complement shifted into the other side of the shift register.


Answer:

input	Present state	Next state	output	Flip-flop	
X	Q(t)	Q(t+1)	Y	J	K
0	0	0	0	0	X
0	1	1	1	X	0
1	0	1	1	1	X
1	1	1	0	X	0

$$J = X$$

$$K = 0$$


$$Y = X \oplus Q$$

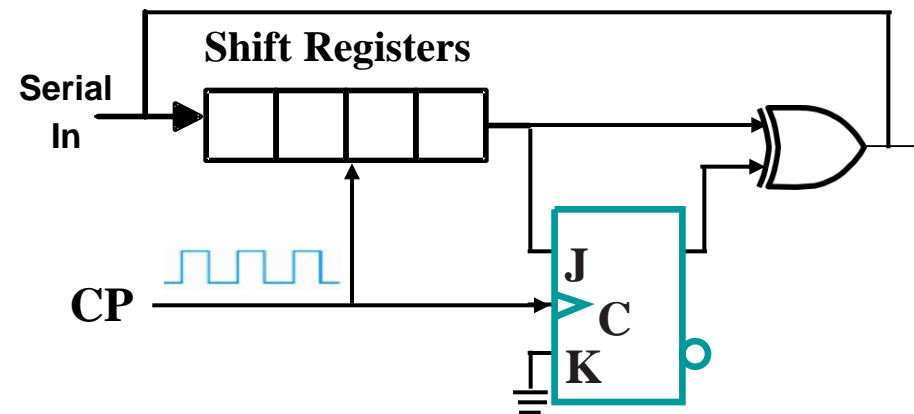

# Chapter 6
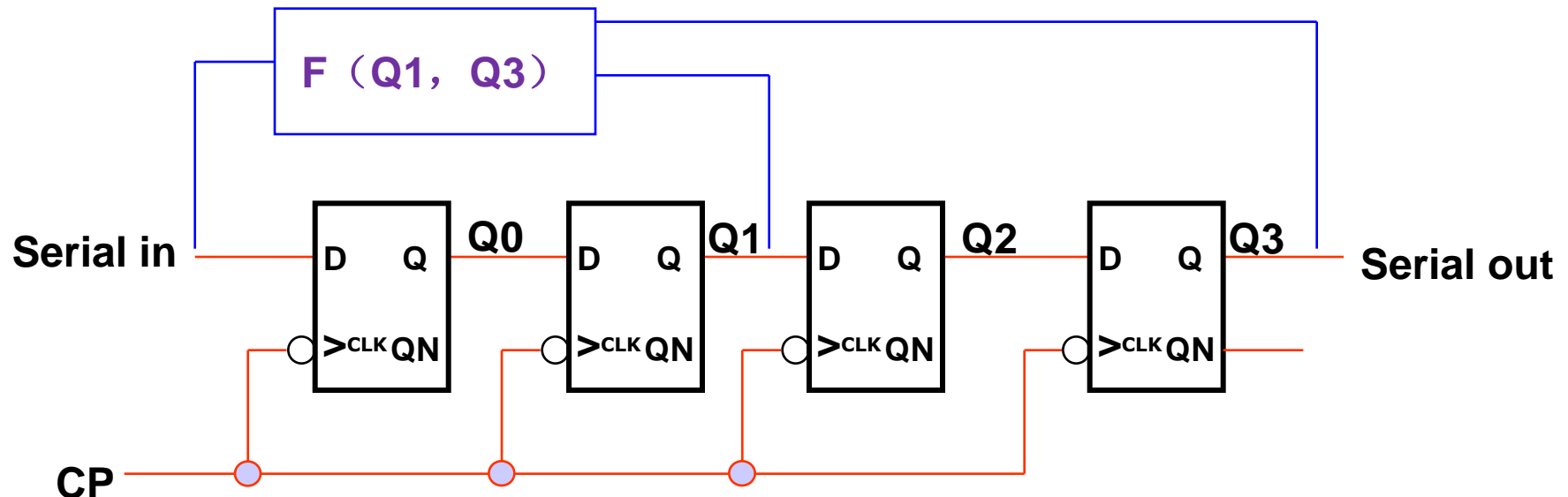
## ■ Problem: Linear-feedback shift register

- A linear feedback shift register (LFSR) is the heart of any digital system that relies on **pseudorandom** bit sequences (PRBS).
- An LFSR is like a black box into which you feed a number, and the generated output is some **linear function of the input** (typically created by some combination of shifting and XOR of the bits).




# Chapter 6
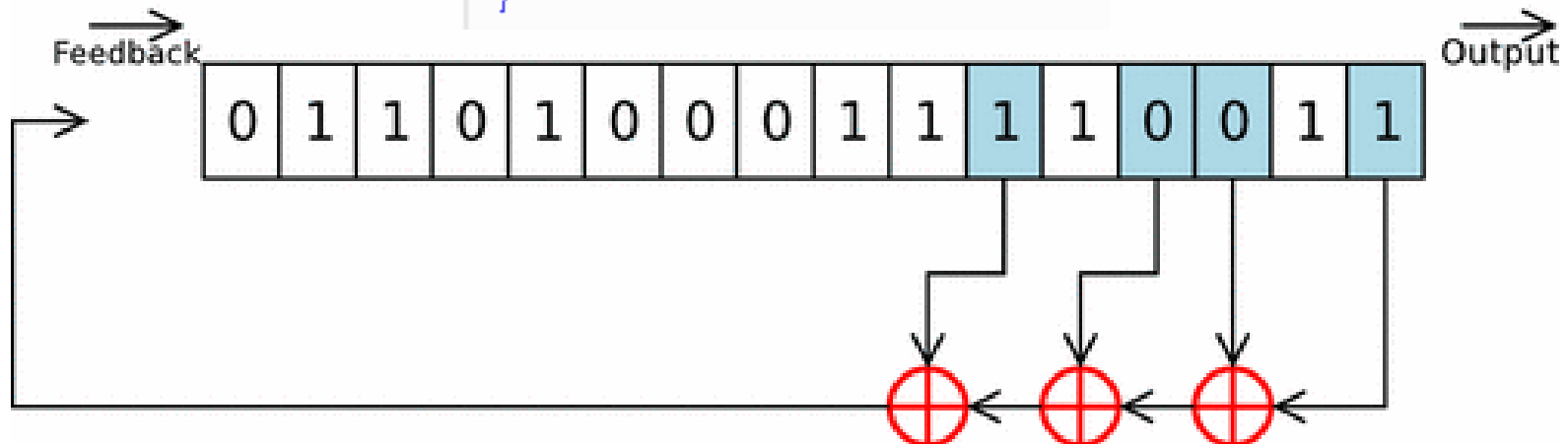
## ■ Problem: Linear-feedback shift register

A linear-feedback shift register (LFSR) is a shift register whose **input bit is a linear function of its previous state**. The initial value of the LFSR is called the **seed**.


```
int main() {  
    int a;  
    srand((unsigned)time(NULL));  
    a = rand();  
    printf("%d\n", a);  
    return 0;  
}
```





# Chapter 6
 
## ■ Problem: Linear-feedback shift register

Design a shift register whose state diagram appears in Figure.



Answer:

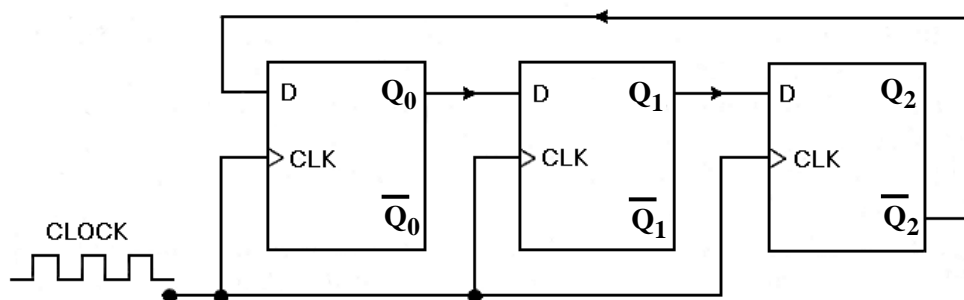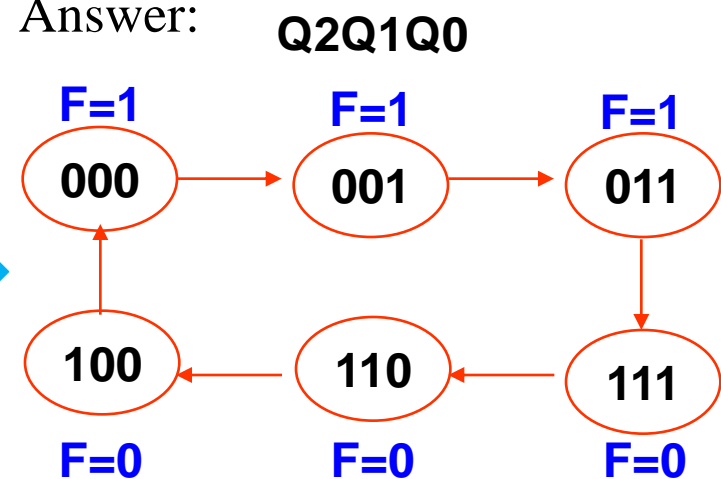

Johnson Counter

$F = \bar{Q}_2$

Q2Q1Q0

Q2Q1Q0 \ F	Q0	
	0	1
00	1	1
01	X	1
11	0	0
10	0	X

# Chapter 6


## ■ Problem: Register Transfer Operations

Two register transfer statements are given (otherwise, R1 is unchanged):

$$C1: R1 \leftarrow R1 + R2$$

$$\overline{C1}C2: R1 \leftarrow R1 - R2$$

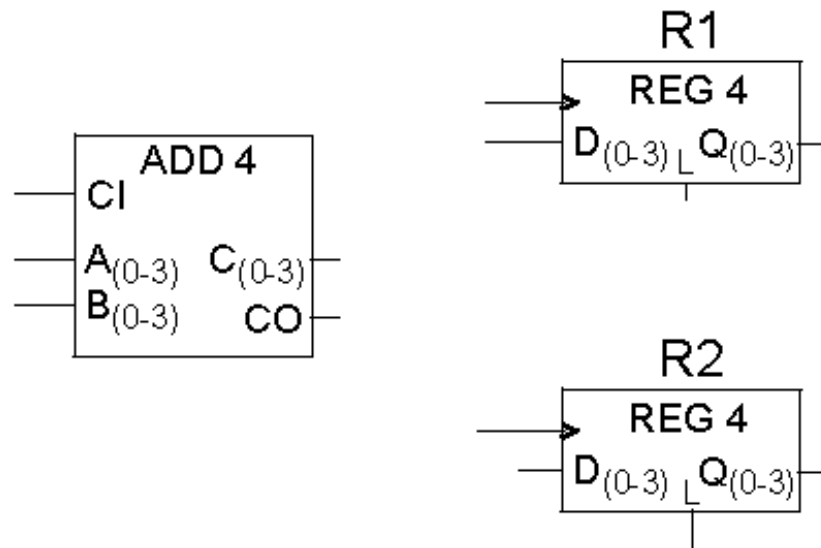Using a 4-bit adder plus external gates as needed. Draw the logic diagram that implements these register transfers.





# Chapter 6

## ■ Problem: Register Transfer Operations

Two register transfer statements are given (otherwise, R1 is unchanged):

$$C1: R1 \leftarrow R1 + R2$$

$$\overline{C1}C2: R1 \leftarrow R1 - R2$$

Using a 4-bit adder plus external gates as needed.

Answer:

### ■ Multiplexer Approach


#### ➤ Load Control

$$\text{Load} = C1 + \overline{C1}C2 \quad \text{for R1}$$

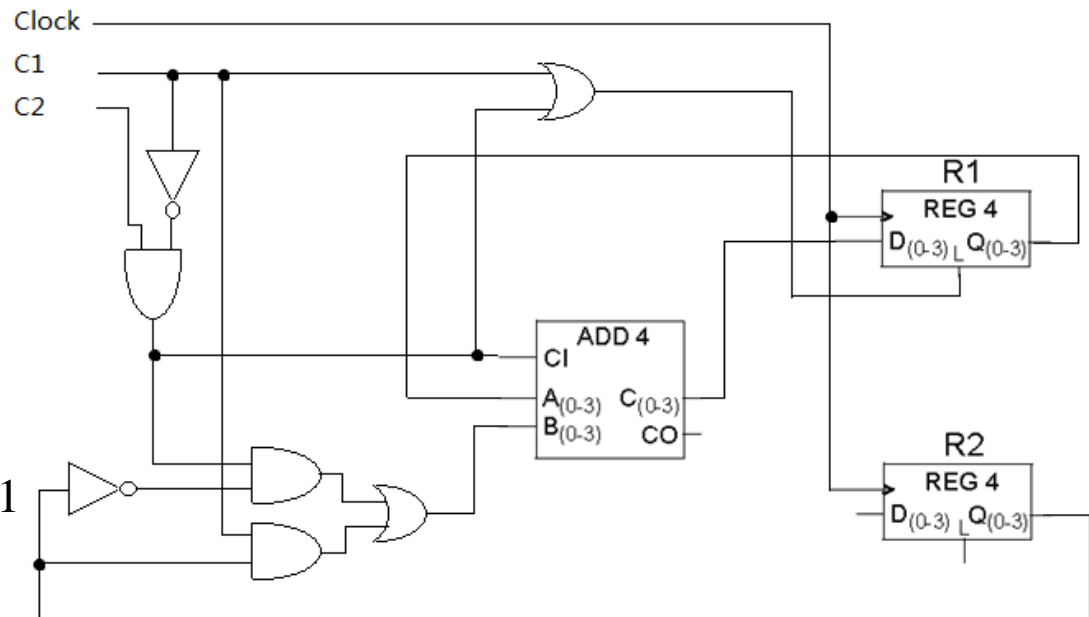
#### ➤ Multiplexer

selection input {  
S0 = C1  
S1 = C2


information input {  
D0 = X  
D1 =  $R1 \leftarrow R1 - R2$      $\overline{C1}C2$     Hold R1  
D2 =  $R1 \leftarrow R1 + R2$     C1



# Chapter 7

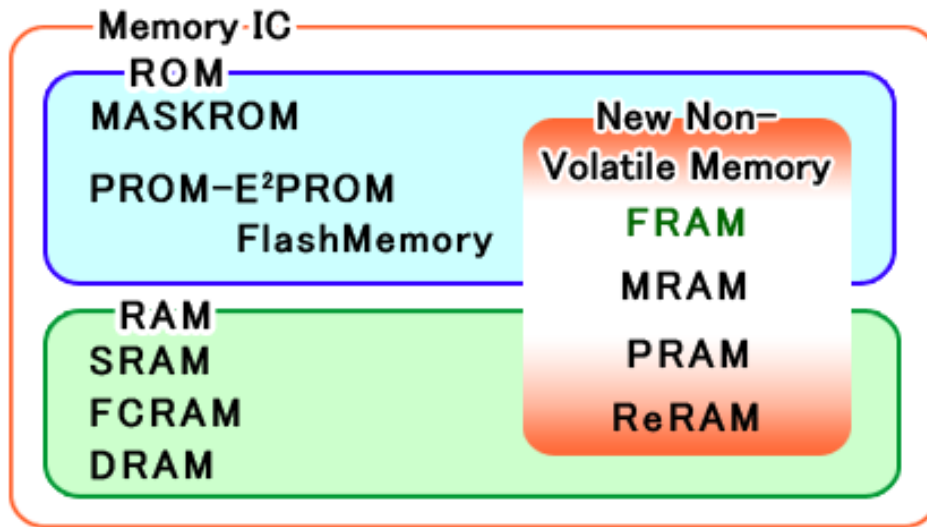

**Computer memory**

 

**Block Diagram of RAM**

# Chapter 7

## ■ Memory Operation Timing

- Read timing
- Write timing

## ■ Coincident Decoding



- Row select
- Column select

## ■ Memory Expansion

- Word-Capacity Expansion: Word extension (address bits are increased)
- Word-Length Expansion: Bit extension
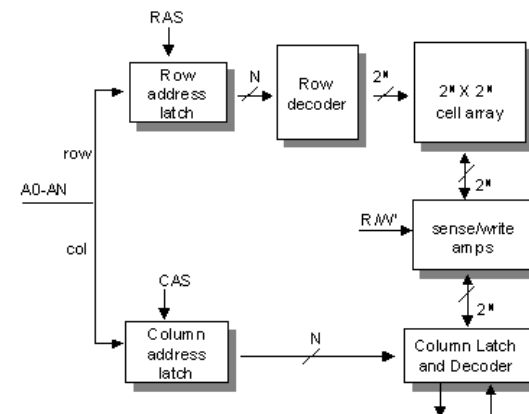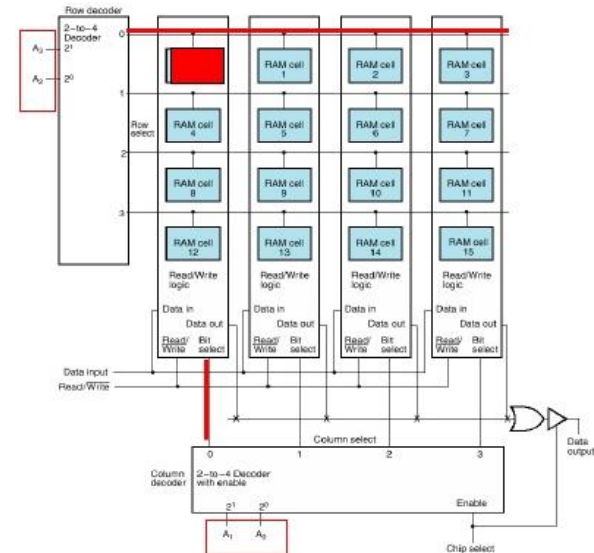
## ■ DRAM

- Address multiplexing
- Refresh policy
- Burst read
- How to calculate memory bandwidth?



# Chapter 7

---

## ■ Problem:

The memory units that follow are specified by the number of words times the number of bits per word. How many address lines and data lines are needed in each case?

- (a)  $8K * 16$                       (b)  $2G * 8$
- (c)  $16M * 32$                     (d)  $256K * 64$

Answer:

- (a)  $8K * 16 = 2^{13} * 16$        $A = 13$   $D = 16$
- (b)  $2G * 8 = 2^{31} * 8$          $A = 31$   $D = 8$
- (c)  $16M * 32 = 2^{24} * 32$      $A = 24$   $D = 32$
- (d)  $256K * 64 = 2^{18} * 64$     $A = 18$   $D = 64$

# Chapter 7

---

## ■ Problem:

A 16K \* 4 memory uses coincident decoding by splitting the internal decoder into X-selection and Y-selection.

- (a) What is the size of each decoder, and how many AND gates are required for decoding the address?
- (b) Determine the X and Y selection lines that are enabled when the input address is the binary equivalent of 6,000.

Answer:

(a)  $16\text{ K} = 2^{14} = 2^7 * 2^7 = 128 * 128$

Each decoder is a 7-to-128-line decoder

Decoders require 256 AND gates, each with 7 inputs

(b)  $(6,000)_{10} = (0101110\ 1110000)_2$

$X = 46, Y = 112$

# Chapter 7

---

## ■ Problem:


A **DRAM** chip uses two-dimensional address multiplexing. It has 13 common address pins, with the row address having one bit more than the column address. What is the capacity of the memory?

Answer:

$13 + 12 = 25$  address lines.


Memory capacity =  $2^{25}$  words.

# Levels of Logic Design

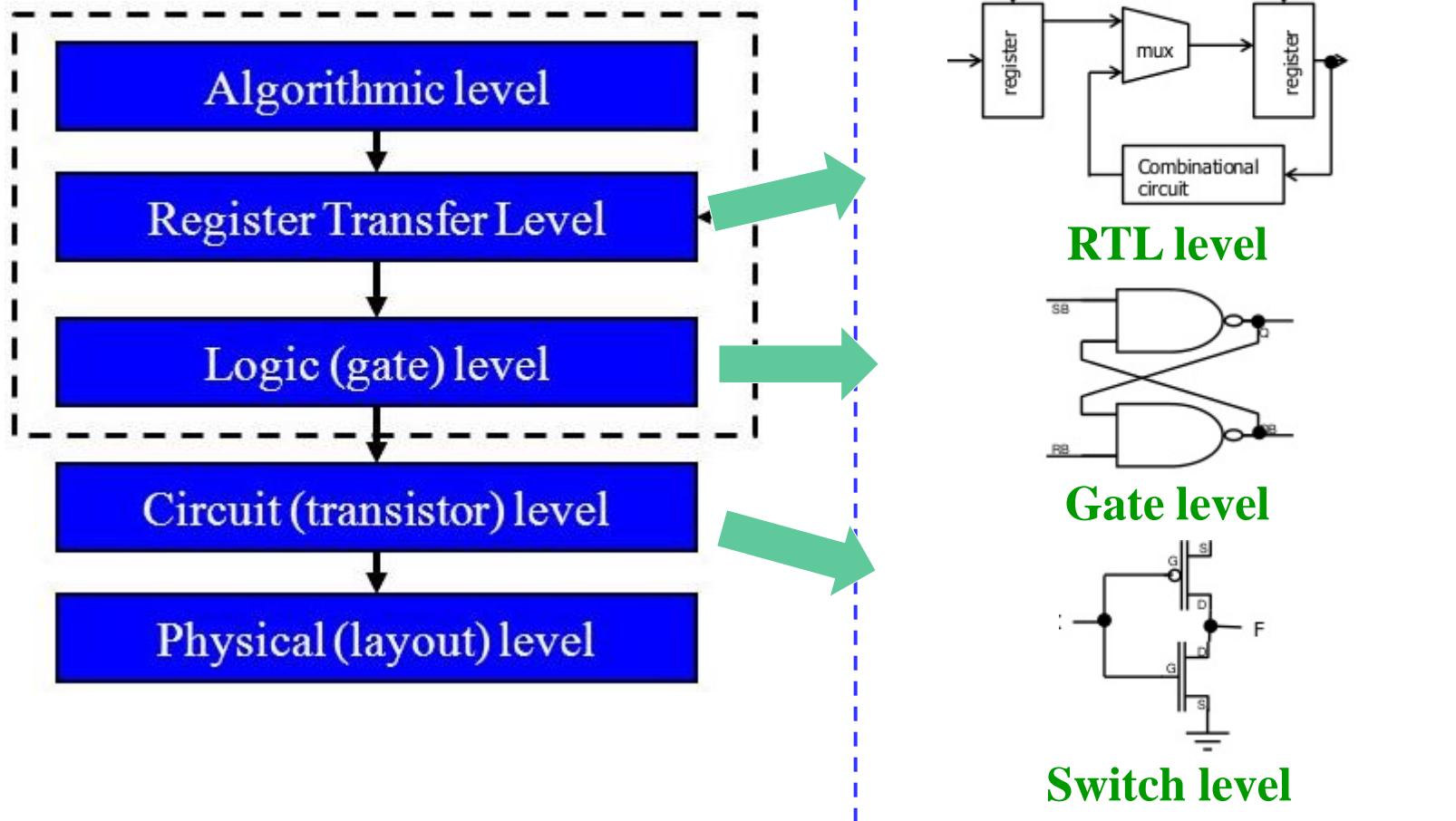
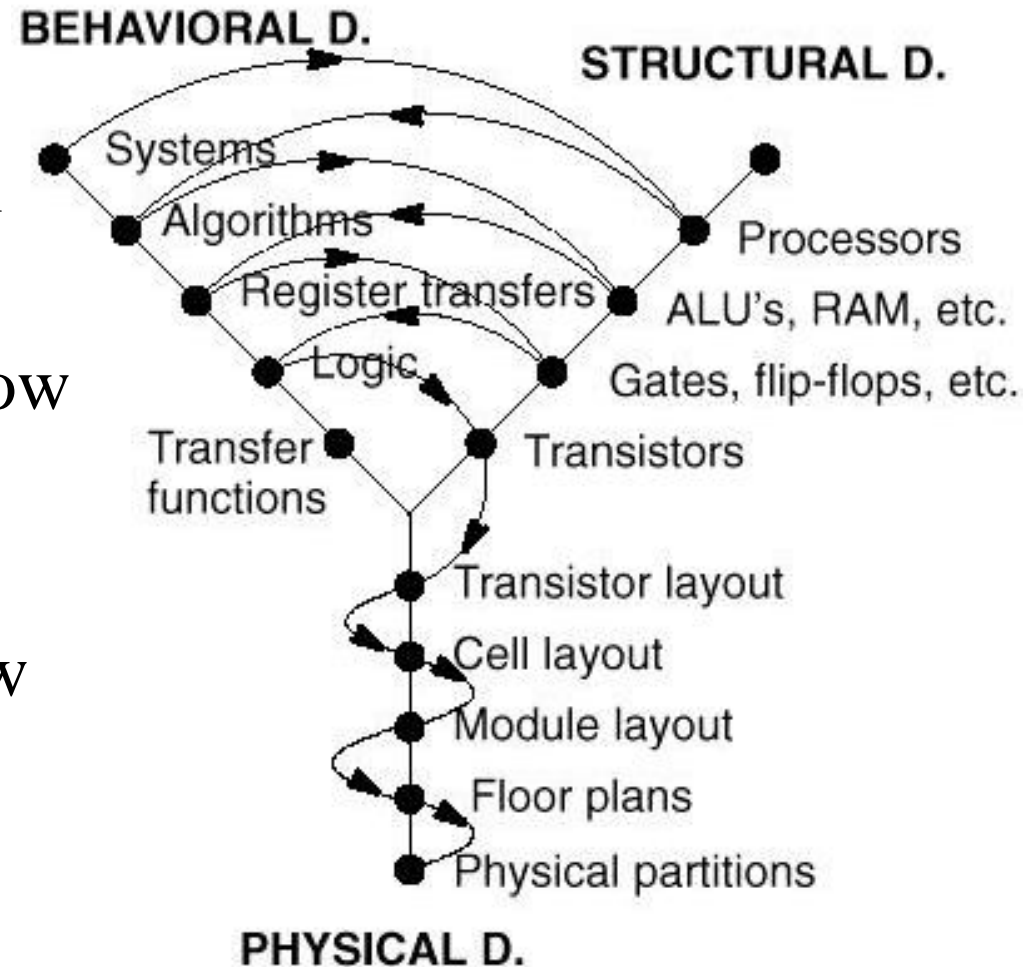
# Levels of Logic Design (continued)

- **Behavioral:** specifies what a specific system does
- **Structural:** specifies how entities are connected together
- **Physical:** specifies how to build a structure





# From Structural Design Perspective

---

- **Gates:** AND, OR, NOT, NAND, NOR, 3-state buffer (Hi-Z), XOR, XNOR
- Gate-Level **Technology Mapping**
- **Rudimentary functions:** decoder, encoder, multiplexer, demultiplexer
- **Arithmetic functions:** half/full adder, ripple carry/carry **lookahead** adder, adder/subtractor, multiplication, shifter, ALU
- **Programmable devices:** PROM, PAL, PLA, FPGA

# From Structural Design Perspective (continued)

---

- **Latches:** SR, JK, D, T
- **Flip-flops:** Master-Slave/Edge-triggered, SR/JK/D/T
- **Registers:** counter, shifter
- **Register Transfer Structures:** MUX-based, MUX bus, 3-state bus
- **Memories:** ROM, SRAM, DRAM, SDRAM

# From Behavioral Design Perspective

---

- Methods of designing combinational circuit
  - Designing theory: time-independent logic
  - Describing methods: truth table (canonical form), timing diagram, boolean function, Karnaugh maps, logic circuit
  - Optimization: two-level circuit optimization (Boolean algebra), iterative array, contraction
  - Timing and performance: gate input cost, fan-in/fan-out, delay model

# From Behavioral Design Perspective (continued)

---

## ■ Methods of designing sequential circuit

- Designing theory: **finite state machine** (Mealy model and Moore model)
- Describing methods: state table, **state diagram**, next state equation(characteristic equation), **input equation**, **excitation equation**, output equation
- Optimization: **state minimization**, **state assignment**
- Timing and performance: glitch, 1's catching,  $t_s$ ,  $t_h$ ,  $t_w$ ,  $t_{px}$

# From Behavioral Design Perspective (continued)

---

## ■ Methods of designing digital system

- Designing theory: register design model, datapath+control unit, state-machine diagram
- Describing methods: Register Transfer Language(RTL)
- Timing and performance: system timing equation  
$$(t_p = t_{\text{slack}} + (t_{\text{pd,FF}} + t_{\text{pd,COMB}} + t_s))$$

## ■ Methods of designing memory

- Describing methods: address, data, operation
- Optimization: coincident decoding, address multiplexing, burst read
- Timing and performance: read timing, write timing, memory bandwidth

# Design Tradeoffs in Logic Circuits

---

## ■ Performance-Cost tradeoff

- Two-level circuit vs. Multiple-level circuit
- Ripple carry vs. Carry lookahead adder
- Parallel adder vs. Serial adder
- Asynchronous counter vs. Synchronous counter
- SRAM vs. DRAM


# Design Tradeoffs in Logic Circuits (continued)

## Performance-Reliability tradeoff

- Latch vs. Flip-flop
- Not encoded (One-hot Code) vs. Encoded (Gray Code)
- Mealy model vs. Moore model
 
## Cost-Reliability tradeoff

- Self-correcting vs. no self-correcting
- Optimal implementation vs. redundant implementation



# End

---

- Tutorial time:

Jan. 11 西1-413

- Final Examination Time:

**Jan. 12, 2019 10:30~12:30**

- Good luck!